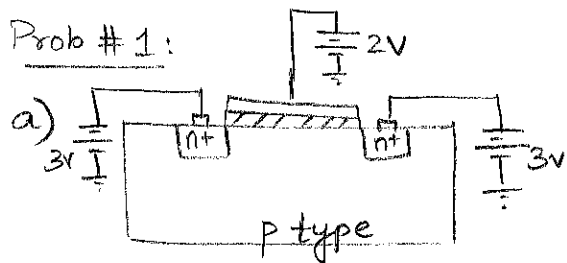


Prob # 1:




$$V_S = 3V, V_G = 2V, V_D = 3V$$

$$\Rightarrow V_{GS} = -1V < V_t \Rightarrow \text{cut off}$$

$$\Rightarrow i_D = 0A$$


b) $V_S = 3V, V_G = 5V, V_D = 3V$

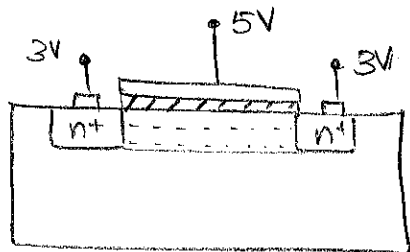

$$V_{GS} > V_t \Rightarrow \text{channel created}$$

$$V_{DS} = 0V \Rightarrow i_D = 0A$$


c) $V_S = 3V, V_G = 5V, V_D = 3.2V$

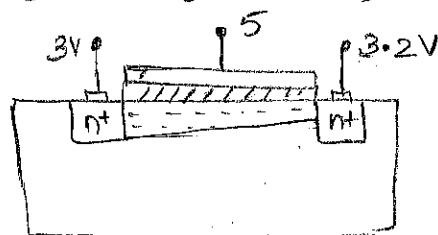

$$V_{GS} > V_t \text{ \& } V_{DS} > 0 \Rightarrow \text{Triode}$$

$$\Rightarrow i_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

d) $V_S = 3V, V_G = 5V, V_D = 4V$

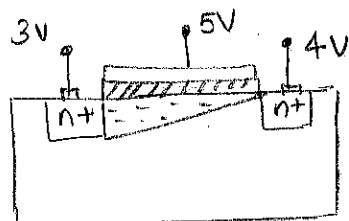


$$V_{GS} - V_t = 5 - 1 = 4V$$

$$V_{DS} = 1V$$

$$V_{DS} = V_{GS} - V_t \Rightarrow \text{pinch off}$$

$$\Rightarrow i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$


e) $V_S = 3V, V_G = 5V, V_D = 8V$

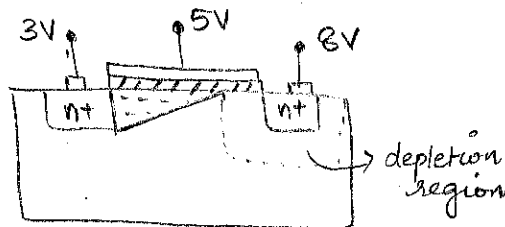


$$V_{DS} > V_{GS} - V_t$$

$$\Rightarrow \text{saturation}$$

$$\Rightarrow i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

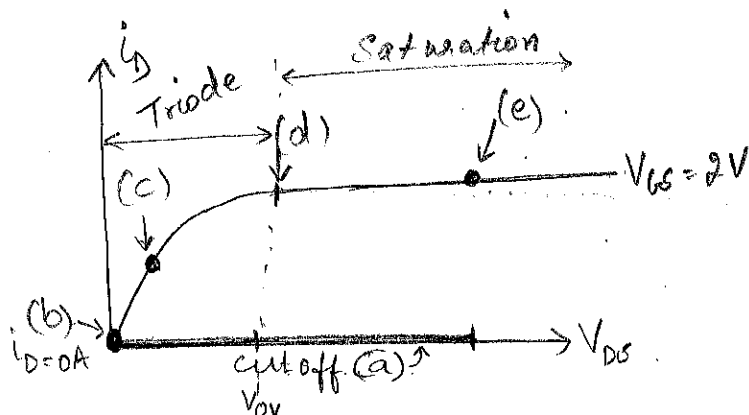

Prob. 2

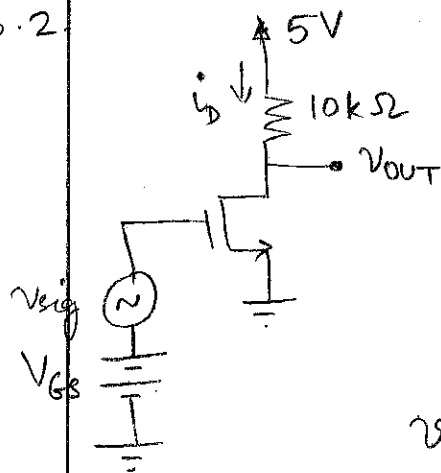


$$k_n = 1 \text{ mA/V}^2$$

$$V_t = 1 \text{ V}$$

$$(V_{GS}, V_{DS})|_{\text{pinchoff}} = (1.9 \text{ V}, 0.9 \text{ V})$$

2 or

5 pts

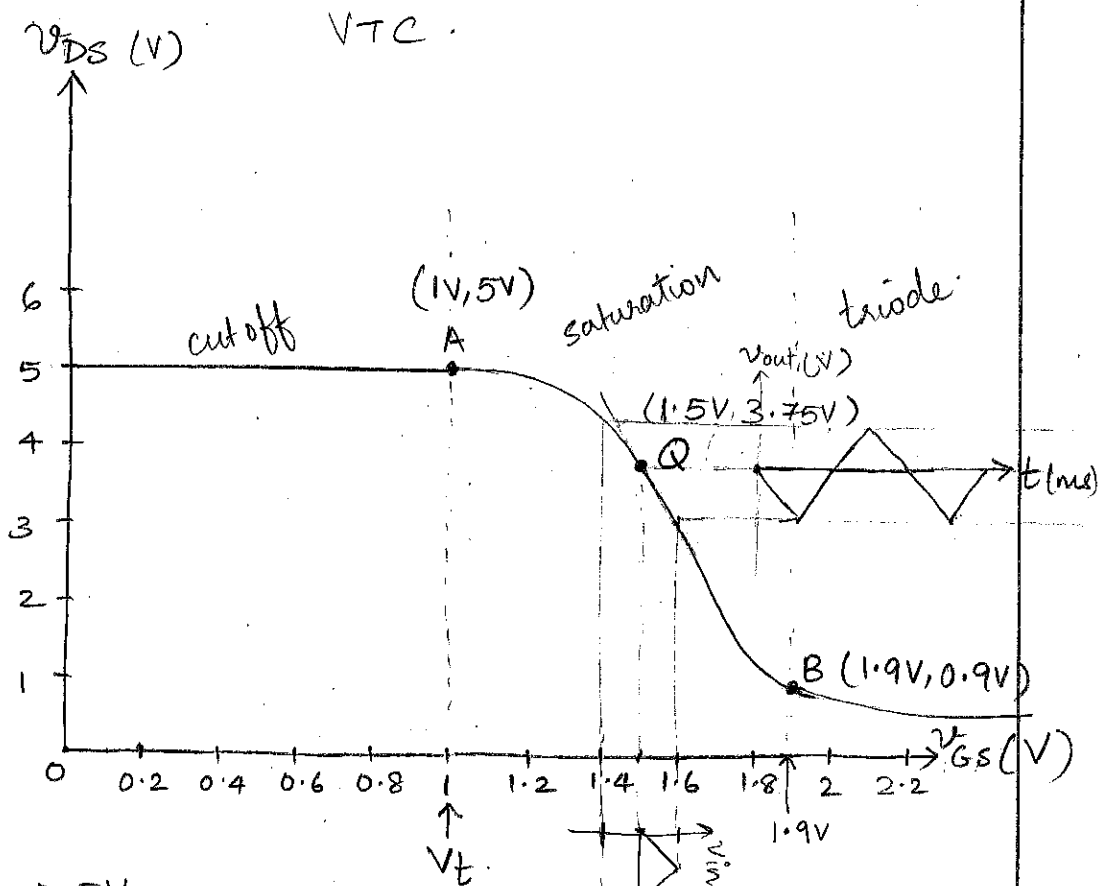

$$Q \text{ pt} \Rightarrow V_{OV} = 0.5 \text{ V}$$

$$\Rightarrow V_{GS} - V_t = 0.5 \text{ V}$$

$$\Rightarrow V_{GS} = \underline{\underline{1.5 \text{ V}}}$$

$$V_{DS} = 5 - I_D R_D$$

$$I_D = \frac{1}{2} \times 1 \text{ m} \times (0.5)^2 = \underline{\underline{0.125 \text{ mA}}}$$

$$\Rightarrow V_{DS} = 5 - 0.125 \text{ m} \times 10 \text{ k}$$

$$= \underline{\underline{3.75 \text{ V}}}$$

$$\text{max o/p swing allowed} \Rightarrow +\text{ve swing} = 5 - 3.75 \text{ V} = 1.25 \text{ V}$$

$$-\text{ve swing} = 3.75 - 0.9 = 2.85 \text{ V}$$

$$\therefore \text{max. allowed swing} = \underline{\underline{1.25 \text{ V}}}$$


attempt = 1

②

②

1 or

⑤

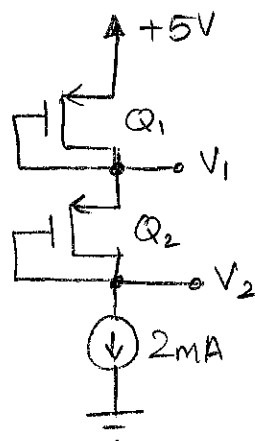

$$V_t = 1V$$

$$k_p = 4mA/V^2$$

$$\lambda = 0.$$

attempt = 1

Both transistors are in saturation:

$$\Rightarrow I_D = \frac{1}{2} k_p (V_{ov})^2.$$

$$I_D = 2mA.$$

$$V_{ov1} = V_{SG1} - V_t = 5 - V_1 - 1 = 4 - V_1$$

$$V_{ov2} = V_{SG2} - V_t = V_1 - V_2 - 1.$$

$$\Rightarrow 2m = \frac{1}{2} \times 4m \times (V_{ov1})^2.$$

$$\Rightarrow (V_{ov})^2 = 1$$

$$\Rightarrow V_{ov} = \pm 1 \quad |V_{ov}| = V_{SG} - V_t \text{ has to be +ve.}$$


$$\textcircled{2} \Rightarrow V_{ov} = +1.$$

$$\textcircled{3} \Rightarrow 4 - V_1 = 1 \Rightarrow \underline{V_1 = 3V}.$$

$$\Rightarrow V_{ov2} = 3 - V_2 - 1 = 2 - V_2.$$

$$\textcircled{3} \Rightarrow 2 - V_2 = 1 \Rightarrow \underline{V_2 = 1V}$$

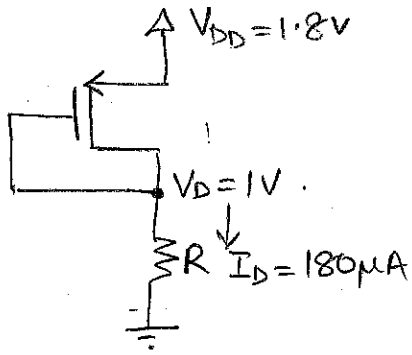\Rightarrow equal drop across Q_1 & Q_2 which makes sense because they have same I_D and hence same V_{ov} . \Rightarrow same $V_{GS} \Rightarrow$ same V_{DS} !



$$V_t = -0.5V \Rightarrow |V_t| = 0.5V$$

$$\mu_p C_{ox} = 100 \mu A/V^2$$

$$L = 0.18 \mu m$$

$$W = ?$$

attempt = ①

③

$$R = \frac{1V}{180 \mu} = \underline{\underline{5.55 k\Omega}}$$

transistor is in saturation \Rightarrow

③


$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - V_t)^2$$

$$\Rightarrow 180 \mu = \frac{1}{2} \times 100 \mu \times \frac{W}{0.18 \mu} (1.8 - 1 - 0.5)^2$$

$$\Rightarrow 180 = \frac{1}{2} \times 100 \times \frac{W}{0.18 \mu} (0.3)^2$$

③
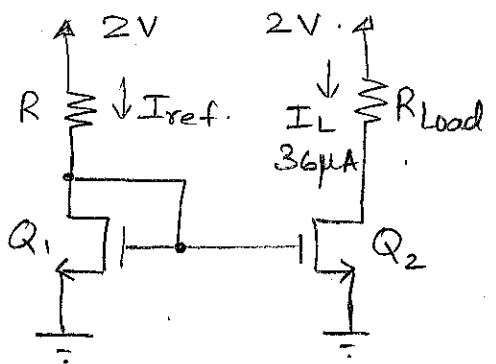
$$\Rightarrow W = \underline{\underline{7.2 \mu m}}$$



$$I_L = 36 \mu A$$

$$V_t = 0.5 V$$

$$\mu_n C_{ox} = 0.4 \text{ mA/V}^2$$

$$\frac{W}{L} = \frac{0.36 \mu}{0.18 \mu}$$

since both transistors are matched and $V_{GS1} = V_{GS2} \Rightarrow I_{ref} = I_L$.

$$\Rightarrow I_{ref} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_t)^2$$

$$\Rightarrow 36 \mu = \frac{1}{2} \times 0.4 \text{ m} \times 2 (V_{GS1} - 0.5)^2$$

$$\Rightarrow V_{GS1} - 0.5 = \sqrt{0.09}$$

$$\Rightarrow V_{GS1} = 0.3 + 0.5 = \underline{\underline{0.8 V}}$$

$$V_{GS1} = V_{DS1} = V_{GS2}$$

$$\Rightarrow V_{DS1} = 0.8 V \Rightarrow V_D = 0.8 V \Rightarrow R = \frac{2 - 0.8}{36 \mu} = \underline{\underline{33.3 k\Omega}}$$

$R_{load \text{ max}} \Rightarrow Q_2$ operates at verge of sat & triode

$$\Rightarrow V_{DS2} = V_{GS2} - V_t$$

$$= 0.8 - 0.5$$

$$= \underline{\underline{0.3 V}}$$

$$\Rightarrow V_D = 0.3 V$$

$$\Rightarrow R_{load \text{ (max)}} = \frac{2 - 0.3}{36 \mu} = \underline{\underline{47.2 k\Omega}}$$


$$\Rightarrow \text{for saturation operation: } 0 < R_{load} \leq \underline{\underline{47.2 k\Omega}}$$

attempt = ①

P#4:

$A_v = -15 \text{ V/V}$
 $I_D = 0.5 \text{ mA}$

Design criteria.

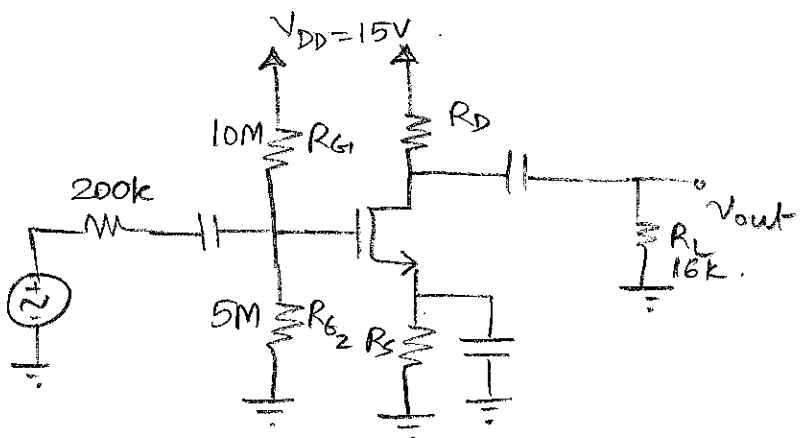


$$V_t = 1 \text{ V}$$

$$k_n = 4 \text{ mA/V}^2$$

$$V_A = 100 \text{ V}$$

DC Analysis:

(2)

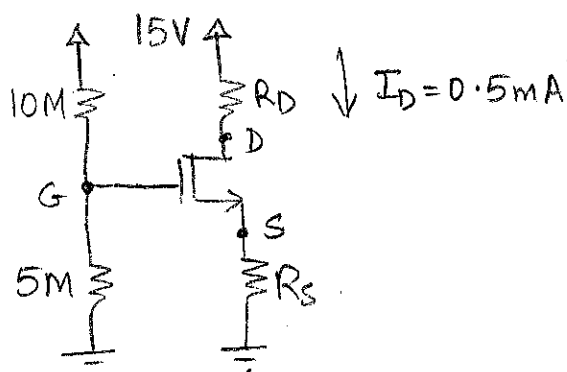

assume saturation operation 'cos it's an amplifier:

$$\Rightarrow I_D = \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$\Rightarrow 0.5 \text{ mA} = \frac{1}{2} \times 4 \text{ mA/V}^2 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = \pm 0.5 \text{ V} \quad \text{for NMOS } (V_{GS} > V_t) \quad V_{ov} \geq 0 \text{ V for it to conduct}$$

$$\Rightarrow V_{ov} = +0.5 \text{ V}$$

$$\Rightarrow V_{GS} - V_t = 0.5 \text{ V}$$

$$(2) \Rightarrow V_{GS} = 0.5 + 1 = \underline{1.5 \text{ V}} \quad \checkmark$$


$$V_G = \frac{5}{5+10} \times 15 = 5 \text{ V} \quad \checkmark$$

$$V_{GS} = V_G - V_S$$

$$\Rightarrow V_S = V_G - V_{GS} = 5 - 1.5 = \underline{3.5 \text{ V}} \quad \checkmark$$

$$\textcircled{3} \Rightarrow R_s = \frac{3.5 - 0}{0.5\text{m}} = \underline{\underline{7\text{k}\Omega}}$$

small signal AC analysis \Rightarrow

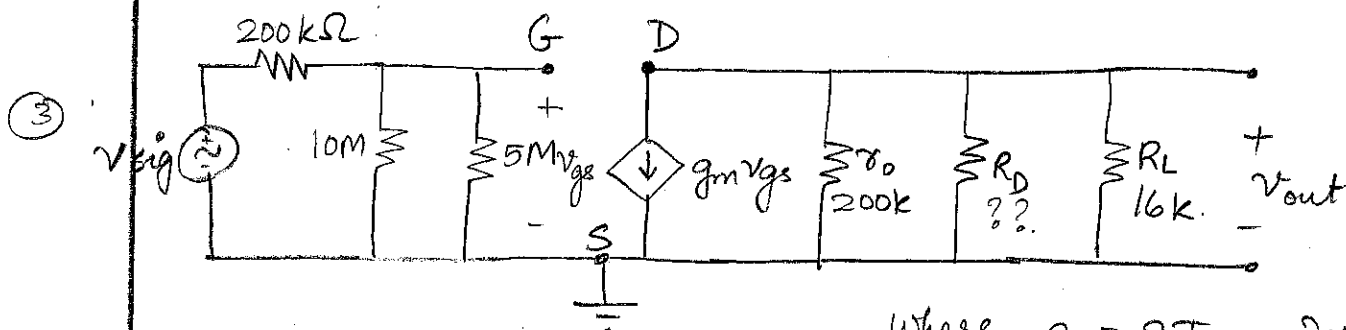

given $A_v = -15 \text{ V/V}$

$$A_v = \frac{v_{out}}{v_{in}}$$

$$v_{out} = -g_m v_{gs} \cdot (r_o \parallel R_D \parallel R_L) \quad \checkmark$$

$$v_{in} = v_{gs}$$

$$\Rightarrow A_v = -g_m (r_o \parallel R_D \parallel R_L)$$

$$\Rightarrow -15 = -2 (200 \parallel 16 \parallel R_D)$$

$$\Rightarrow 7.5\text{k} = 14.81\text{k} \parallel R_D$$

$$\Rightarrow \frac{1}{R_D} = \frac{1}{7.5\text{k}} - \frac{1}{14.81\text{k}}$$

$$\textcircled{3} \Rightarrow R_D = \underline{\underline{15.2\text{k}\Omega}} \quad \checkmark$$

$$G_v = \frac{v_{out}}{v_{sig}} = \frac{v_{out}}{v_{in}} \cdot \frac{v_{in}}{v_{sig}}$$

$$v_{in} = v_{gs} = \frac{3.33\text{M}}{3.33\text{M} + 0.2\text{M}} v_{sig} \\ = \underline{\underline{0.94}}$$

$$(10\text{M} \parallel 5\text{M} = 3.33\text{M})$$

$$\textcircled{2} \Rightarrow G_v = -15 \times 0.94 \quad \checkmark \\ = \underline{\underline{14.1 \text{ V/V}}}$$

assumed saturation

$$\rightarrow \text{verify} \Rightarrow V_{DS} \geq V_{GS} - V_t$$

$$V_{GS} - V_t = V_{OV} = \underline{0.5V}$$

$$V_D = 15 - I_D \cdot R_D$$

$$= 15 - 0.5\text{mA} \times 15.2\text{k}\Omega$$

$$= \underline{7.4V}$$

$$V_{DS} = V_D - V_S$$

$$= 7.4 - 3.5$$


$$= \underline{3.9V} \quad (3.9V > 0.5V)$$

$\Rightarrow V_{DS}$ is greater than V_{OV} , hence valid assumption.

②

P#5: For impedance matching, we need a CG amplifier where R_{in} of the amplifier equals R_{sig} .

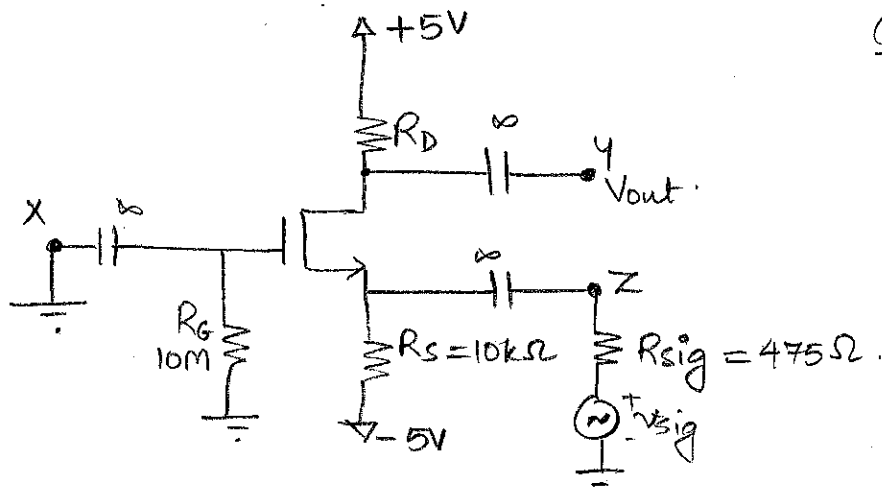(2pt) CG config \Rightarrow $X = GND$, $Z = Input$, $Y = output$.




Given:

$$V_{ov} = 0.4V$$

$$V_{DS} = V_{ov} + 0.8V = \underline{\underline{1.2V}}$$

Small signal AC model \Rightarrow

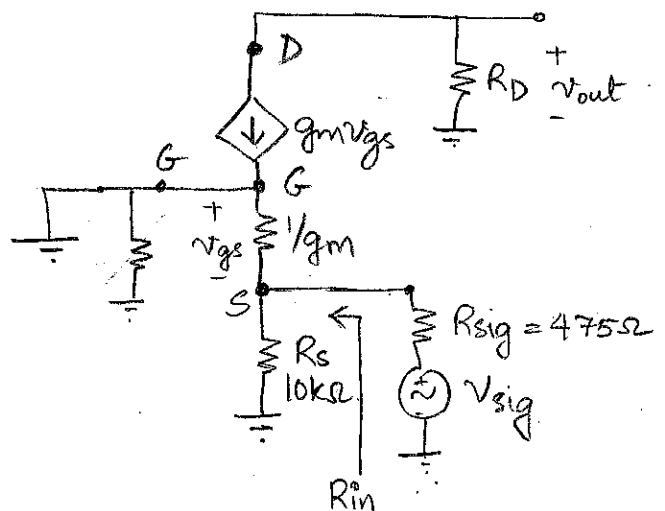

for impedance matching,


$$R_{in} = R_{sig} = \underline{\underline{475\Omega}}$$

(2pt)

To determine R_{in} :

- 1) disconnect input signal source.
- 2) $R_{in} = R_{b/w S \text{ and } GND}$.
- 3) current source has ∞ resistance.

\Rightarrow

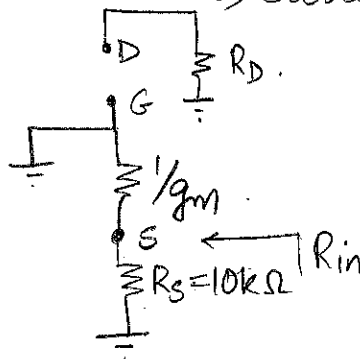

$$\Rightarrow R_{in} = \frac{1}{g_m} \parallel R_S$$

$$\Rightarrow \frac{1}{475} = g_m + \frac{1}{10000}$$

$$\Rightarrow g_m = \underline{\underline{2mA/V}}$$

(3pt)

To find the resistor values, we need the DC bias current, I_D .


$$g_m = \frac{2I_D}{V_{ov}}$$

$$\Rightarrow 2 \text{ mA/V} = \frac{2 \times I_D}{0.4 \text{ V}}$$

$$\Rightarrow I_D = \underline{\underline{0.4 \text{ mA}}}$$

Now, perform DC analysis to find the value of R_D .

DC Analysis:

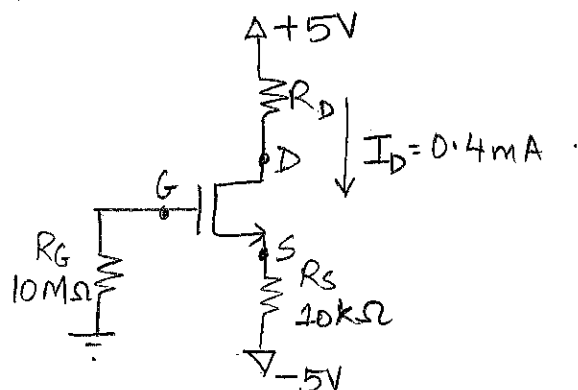

$$V_S = I_D R_S - 5 = (0.4 \text{ mA})(10 \text{ k}) - 5 = \underline{\underline{-1 \text{ V}}}$$

$$V_{GS} = 1 \text{ V} \text{ and } V_{ov} = 0.4 \text{ V given.}$$

$$V_{DS} = V_{ov} + 0.8 \text{ V} = 1.2 \text{ V}$$

$$\Rightarrow V_D = 1.2 + V_S$$

$$= \underline{\underline{0.2 \text{ V}}}$$

$$R_D = \frac{5 - 0.2}{0.4 \text{ mA}} = \underline{\underline{12 \text{ k}\Omega}} \Rightarrow R_D \leq \underline{\underline{12 \text{ k}\Omega}}$$

if $R_D > 12 \text{ k}\Omega \Rightarrow V_D < 0.2 \text{ V}$ and the output swing would reduce from 0.8 V .