

P#9.64


2

Please provide your ans. in sinusoidal form

1. If $v_g = 75\cos 5000t$ V in the following circuit, find i_Δ using Mesh Analysis Method.

[20 points]

(10pts for anything reasonable)

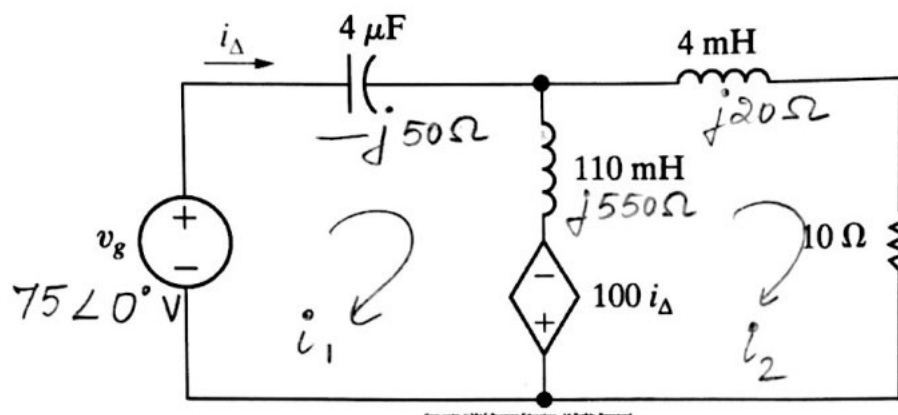

5pts for conversion into freq domain

5pts (3 for any final ans.)

$$i_\Delta = 2.55 \angle 78.7^\circ \text{ A}$$

mesh 1:

$$-75 - j50 \cdot i_1 + j550 (i_1 - i_2) - 100 i_1 = 0$$

$$\Rightarrow i_1 (-100 + j500) + i_2 (-j550) = 75 \quad \text{--- (1)}$$

mesh 2:

$$j20 i_2 + 10 i_2 + 100 i_1 + j550 (i_2 - i_1) = 0$$

$$\Rightarrow i_1 (100 - j550) + i_2 (10 + j570) = 0 \quad \text{--- (2)}$$

10 pts.

$$\Rightarrow i_2 = \frac{i_1 (-100 + j550)}{10 + j570}$$

substituting in (1) \rightarrow

$$i_1 (-100 + j500) + i_1 \left(\frac{-100 + j550}{10 + j570} \right) (-j550) = 75$$

Page intentionally left blank. You may use this page for your work.

$$\Rightarrow i_1 (-100 + j500)(10 + j570) + i_1 (-100 + j550)(-j550) = 75(10 + j570)$$

$$\Rightarrow i_1 (-1000 + j5000 - j57000 - 285000 + j55000 + 302500) = 750 + j42750$$

$$\Rightarrow i_1 (16500 + j3000) = 750 + j42750$$

$$\Rightarrow i_1 = \frac{42756.6 \angle 88.99^\circ}{16770.5 \angle 10.3^\circ}$$

$$= \underline{\underline{2.55 \angle 78.7^\circ \text{ A}}} = 0.5 + j2.5$$

$$i_2 = i_1 \left(\frac{-100 + j550}{10 + j570} \right) = \frac{(2.55 \angle 78.7^\circ)(559 \angle 100.3^\circ)}{570.09 \angle 88.99^\circ}$$


$$= \underline{\underline{2.5 \angle 90^\circ \text{ A}}}$$

$$\Rightarrow V_o = 10 i_2 = \underline{\underline{25 \angle 90^\circ \text{ V}}}$$

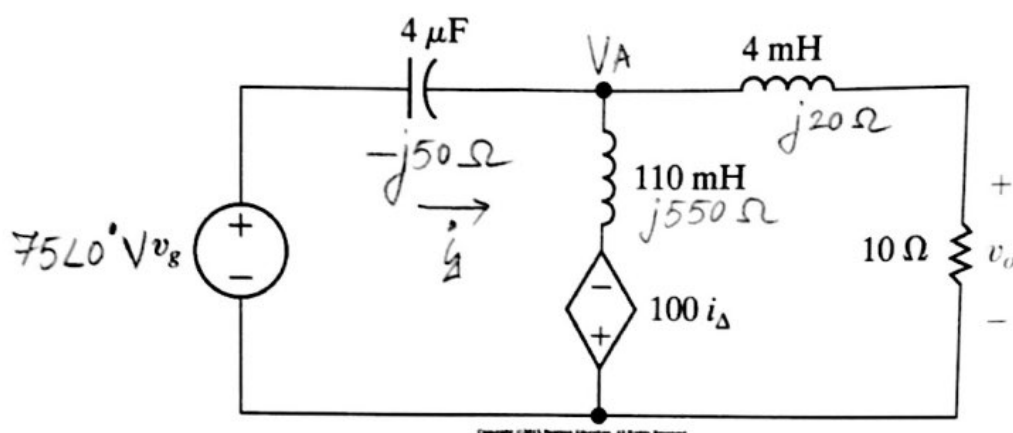2. If $v_g = 75\cos 5000t$ V in the following circuit, find v_o using Node Analysis Method.

[20 points]

all eq correct.
= 15 pts
+ final wrong ans = 2 pts



$$v_o = 25 \angle 90^\circ \text{ V}$$

KCL @ node A \rightarrow

$$\frac{V_A - 75}{-j50} + \frac{V_A + 100i_\Delta}{j550} + \frac{V_A}{10 + j20} = 0 \quad \text{--- 10 pts}$$

$$\Rightarrow \frac{V_A j - j75}{+50} + \frac{jV_A + j100i_\Delta}{-550} + \frac{V_A 10 - j20V_A}{100 + 400} = 0$$

$$\Rightarrow \frac{j11V_A - j825}{11} + \frac{-jV_A - j100i_\Delta}{10} + \frac{10V_A - j20V_A}{10} = 0$$

$$\Rightarrow j11V_A - j825 - jV_A - j100i_\Delta + 11V_A - j22V_A = 0$$

$$\Rightarrow V_A(11 - j12) - j825 + j100\left(\frac{75 - V_A}{-j50}\right) = 0$$

$$\Rightarrow V_A(11 - j12) - j825 + 150 - 2V_A = 0 \quad \rightarrow i_\Delta \text{ (5 pts)}$$

Page intentionally left blank. You may use this page for your work.

$$\Rightarrow V_A (9 - j12) = -150 + j825$$

$$\Rightarrow V_A = \frac{-150 + j825}{9 - j12}$$

$$= \frac{838.5 \angle 100.3^\circ}{15 \angle -53.13^\circ}$$

$$= \underline{\underline{55.9 \angle 153.4^\circ \text{ V}}} \quad \text{--- 5 pts.}$$

$$V_o = \frac{V_A}{10 + j20} \times 10$$

$$= \frac{10 V_A (10 - j20)}{10^2 + 20^2}$$

$$= \frac{V_A (1 - j2)}{5}$$

$$= \frac{(55.9 \angle 153.4^\circ)(2.24 \angle -63.4^\circ)}{5}$$




$$= \underline{\underline{25 \angle 90^\circ \text{ V}}} \quad \text{--- 5 pts.}$$

(total 10 for even attempting anything reasonable)

P# 9.45

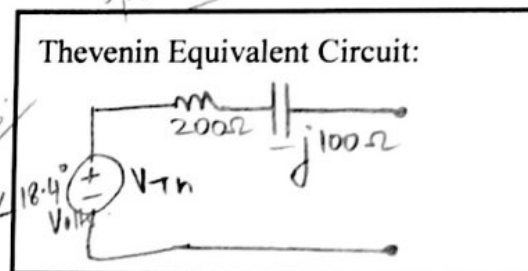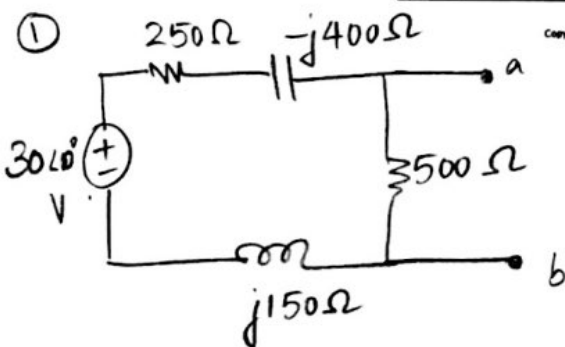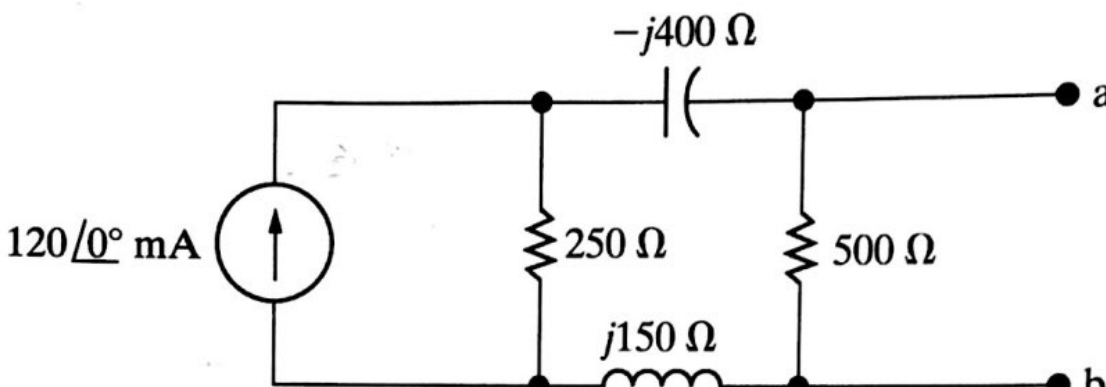
3. For the circuit shown below:

- ✓ A. Draw the Thevenin equivalent circuit, with respect to terminals a & b. [20 points] (10 pts for attempt)
- ✓ B. Find the load impedance required for maximum power transfer. [5 points]
- C. Find the maximum average power delivered to the load. [5 points]



$Z_{Th} = 5 \text{ pts}$ $Z_{Load} = 200 + j100 \Omega$

$P_{max} = 0.225 \text{ W}$

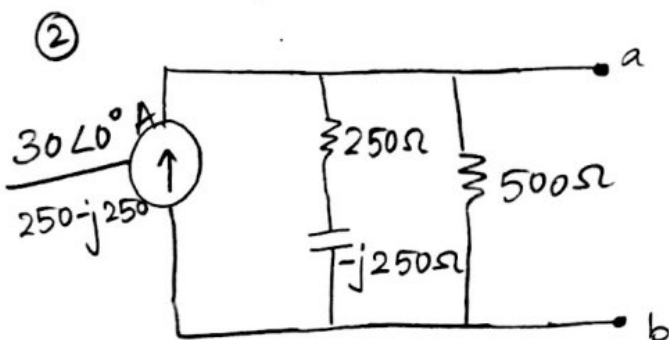

$Z_{Th} = (250 - j250) \parallel 500$

$$= \frac{(250 - j250)(500)}{250 - j250 + 500}$$

$$= \frac{125000(1 - j)}{250(3 - j)}$$

$$= 500 \frac{(1 - j)(3 + j)}{9 + 1}$$

$$= 50(3 - j3 + j + 1)$$

$$= 50(4 - j2)$$

5 pts for sub circuit

5 pts

18.97∠-18.4° V

200 - j100 Ω

500(353.5∠-45°)

790.6∠-18.4°


223.56∠-26.6°

200 - j100 Ω

Page intentionally left blank. You may use this page for your work.

$$\Rightarrow Z_{Th} = \underline{200 - j100 \Omega}$$

(3)

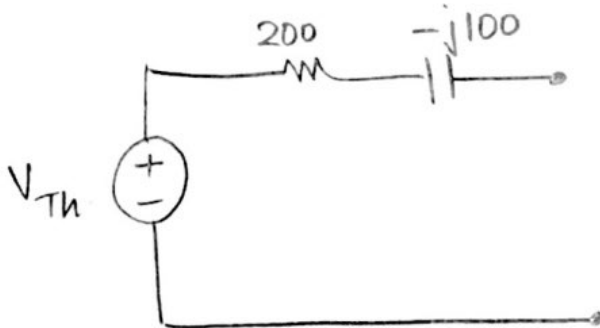

$$\begin{aligned} V_{Th} &= \frac{30 \angle 0^\circ}{250 - j250} \times (200 - j100) \\ &= \frac{30 \angle 0^\circ}{353.5 \angle 45^\circ} (223.6 \angle -26.6^\circ) \\ &= \underline{\underline{18.97 \angle +18.4^\circ \text{ V}}} \end{aligned}$$

$$Z_{load} = Z_{Th}^* = \underline{\underline{200 + j100 \Omega}}$$



$$\begin{aligned} P_{max} &= \frac{V_{Th_{RMS}}^2}{4 R_{Th}} = \frac{\left(\frac{18.97}{\sqrt{2}} \right)^2}{4 \times 200} \\ &= \underline{\underline{0.225 \text{ W}}} \end{aligned}$$

- 5 pts if they used RMS & correct equation & unit.

P#10.33

→ Please include the correct units.

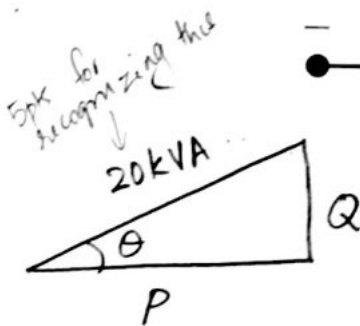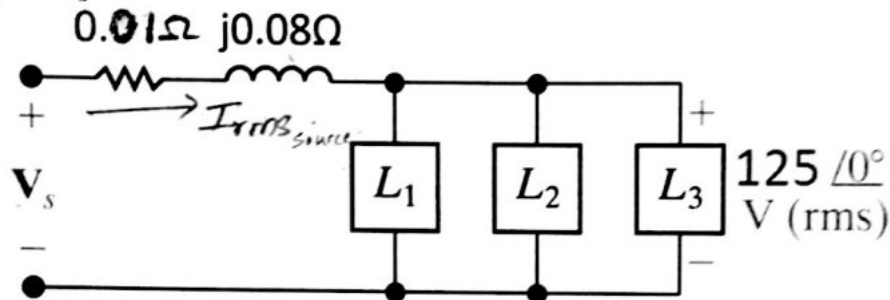4. A group of appliances require a total of 20kVA at 0.85 pf lagging, when operated at 125Vrms and 60Hz. The impedance of the line supplying the appliances is $0.01 + j0.08 \Omega$.
- Draw the power triangle showing the apparent, average and reactive power required by the group of appliances. [10 points]
 - Find the capacitor (in mF) that needs to be connected across the load to improve the load power factor to unity. [10 points]
 - Find the average power loss in the line **before and after** the capacitor is added. [10 points]



$$C = 1.79 \text{ mF}$$

$$(\text{before adding } C) P_{\text{loss}} = 256 \text{ W}$$


$$(\text{after adding } C) P_{\text{loss}} = 185 \text{ W}$$

$$\cos \theta = 0.85 \Rightarrow \theta = 31.78^\circ$$

$$P = S \cos \theta = (20 \text{ k}) \times 0.85 = 17 \text{ kW}$$

$$Q = S \sin \theta = 10.53 \text{ kVAR}$$

Load Power Triangle:

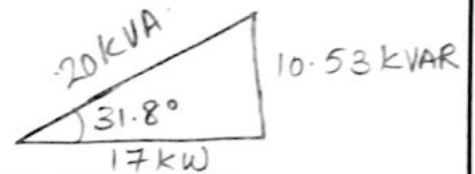

capacitor needs to provide -10.53 kVAR . — 5pt

$$\Rightarrow Q = -10.53 \text{ kVAR}$$

$$Q = \frac{V_{\text{rms}}^2}{X} = -10.53 \text{ kVAR} \dots 3 \text{ pts}$$

$$\Rightarrow X_c = \frac{125^2}{-10.53 \text{ k}} = -1.48$$

Page intentionally left blank. You may use this page for your work.

$$\Rightarrow Z_C = -j1.48 \, \Omega$$

$$= \frac{-j}{\omega C}$$

$$\Rightarrow C = \frac{1}{2\pi \times 60 \times 1.48} = 0.001792 \, F$$

$$= \underline{\underline{1.79 \, mF}} \quad \text{--- 2pts}$$

$$S = V_{rms} I_{rms}^*$$

Before

$$S_1 = 20 \angle 31.78^\circ \, kVA = (125 \angle 0^\circ)(I_{rms} \angle -\theta_i)$$

$$\Rightarrow I_{rms} \angle -\theta_i = 160 \angle 31.78^\circ \quad \text{--- 3pts}$$

$$\Rightarrow I_{rms} \angle \theta_i = 160 \angle -31.78^\circ \, A$$

$$P_{loss} = I_{rms}^2 \times R = 160^2 \times 0.01 = \underline{\underline{256 \, W}} \quad \text{--- 2pts}$$

After


$$S_2 = 17 \angle 0^\circ \, kVA = (125 \angle 0^\circ)(I_{rms} \angle -\theta_i)$$

$$\Rightarrow I_{rms} \angle \theta_i = 136 \angle 0^\circ \, A \quad \text{--- 3pts}$$

$$P_{loss} = I_{rms}^2 R = 136^2 \times 0.01 = \underline{\underline{185 \, W}} \quad \text{--- 2pts}$$

AP # 9.15
w/ modified dot convention.

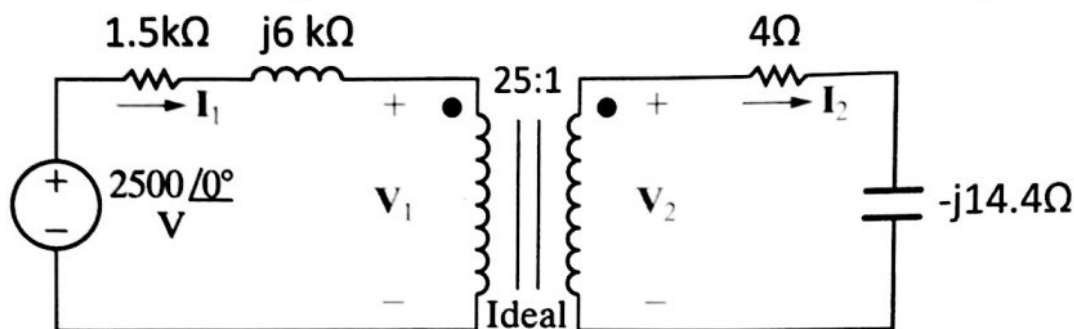5. For the following circuit containing ideal transformer, find V_2 and I_2 . [Bonus 10 points]



$$\textcircled{1} -2500 + (1.5k + j6k)I_1 + V_1 = 0$$

$$\textcircled{2} -V_2 + (4 - j14.4)I_2 = 0$$

$V_2 =$ ~~_____~~

5pts. $I_2 = \underline{\underline{12.5 \angle +36.8^\circ \text{ A}}}$

$$\frac{V_1}{V_2} = \frac{I_2}{I_1} = \frac{25}{1}$$

$$\Rightarrow V_1 = 25V_2 \quad I_1 = I_2/25 \quad \text{--- 4pts.}$$

$$\Rightarrow \textcircled{1} \rightarrow -2500 + (1500 + j6000) \frac{I_2}{25} + 25V_2 = 0$$

$$\Rightarrow -2500 + (60 + j240)I_2 + 25(4 - j14.4)I_2 = 0$$

$$\Rightarrow I_2(60 + j240 + 100 - j360) = 2500$$

$$\Rightarrow I_2 = \frac{2500}{160 - j120} = \frac{2500 \angle 0^\circ}{200 \angle -36.8^\circ} = \underline{\underline{12.5 \angle +36.8^\circ \text{ A}}}$$