

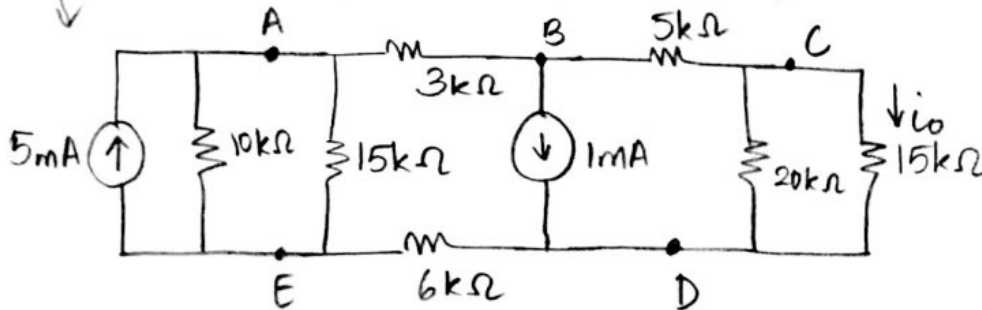
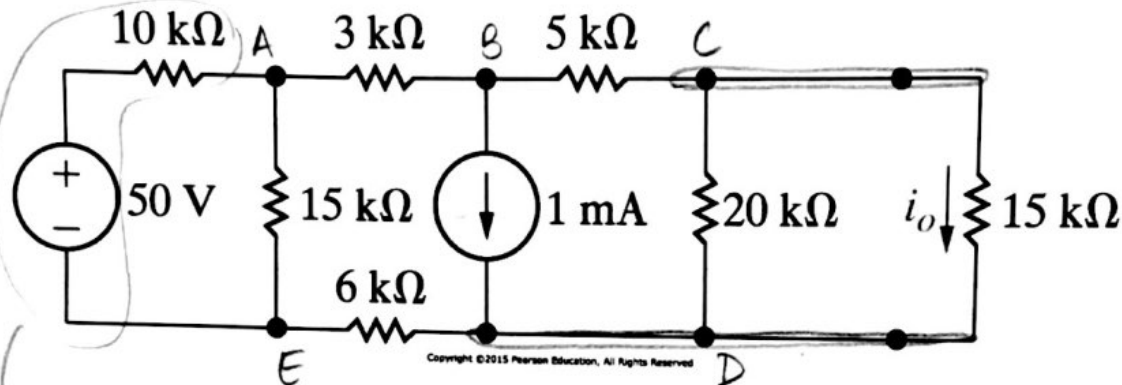
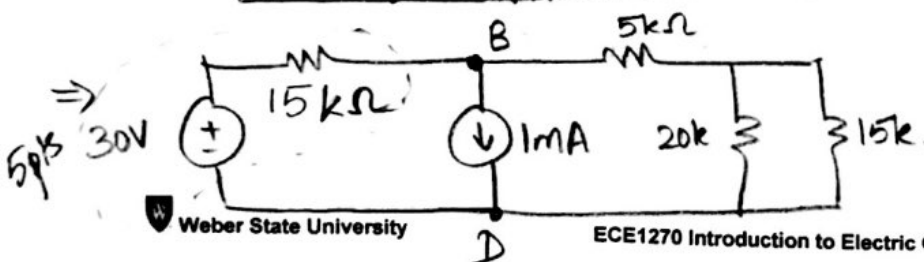


-4 for every conversion w/o a resistor.






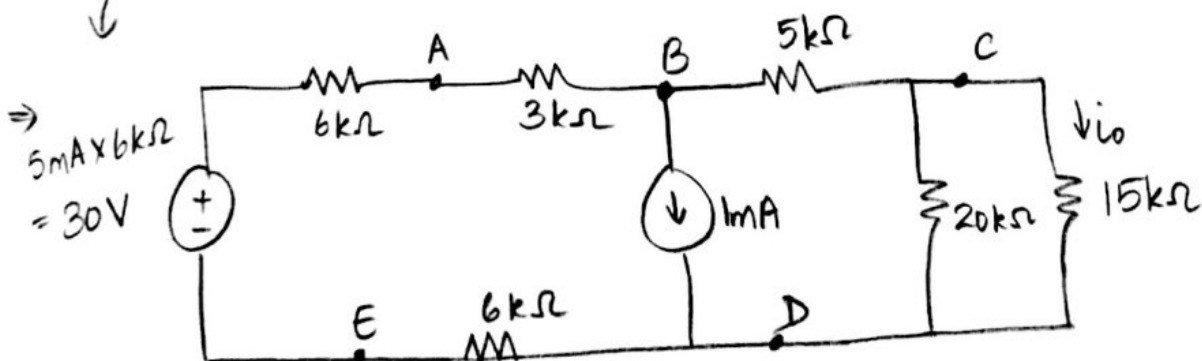
1. Using a series of source transformations, simplify the circuit and determine the current i_o . Please make sure to draw out each subsequent circuit. [25 points]



$$i_o = 0.3 \text{ mA}$$

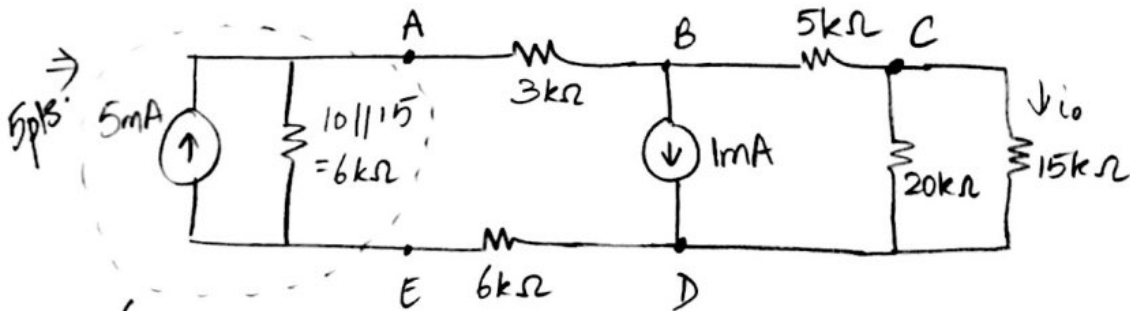

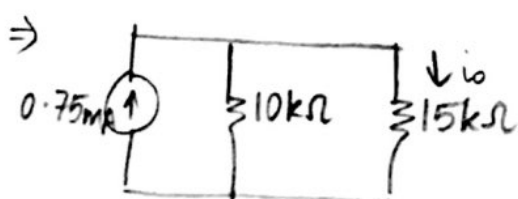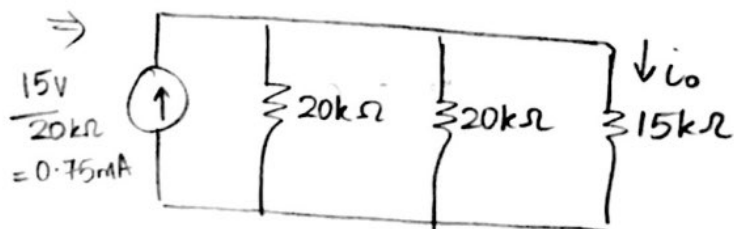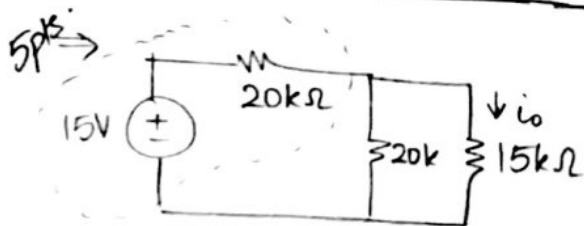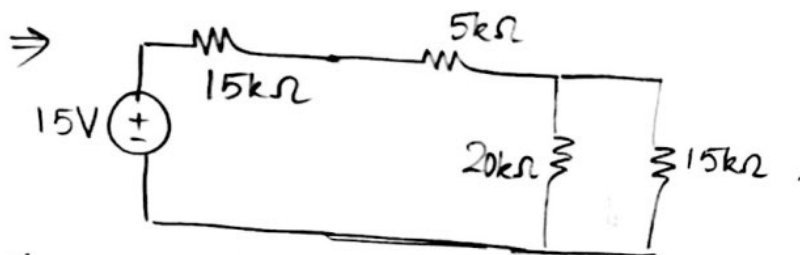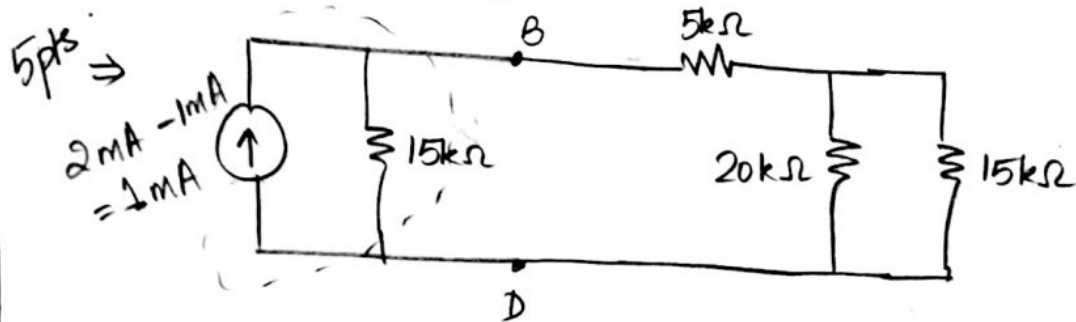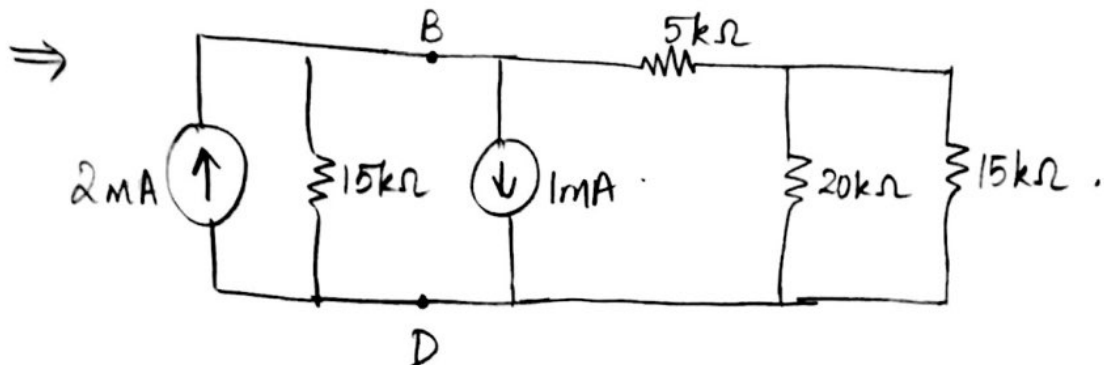Page intentionally left blank. You may use this page for your work.




⇒ $i_o = 0.75\text{mA} \left(\frac{6\text{k}\Omega}{15\text{k}\Omega} \right)$ 5pts.

$= 0.3\text{mA}$

2. A) Draw the Thevenin Equivalent with respect to terminals a,b for the circuit shown.
 B) Draw the Norton Equivalent with respect to terminals a,b for the circuit shown.
 C) Find the maximum power delivered by the circuit.

Please show all your intermediate circuits and separate your work into sections.

[25 points]

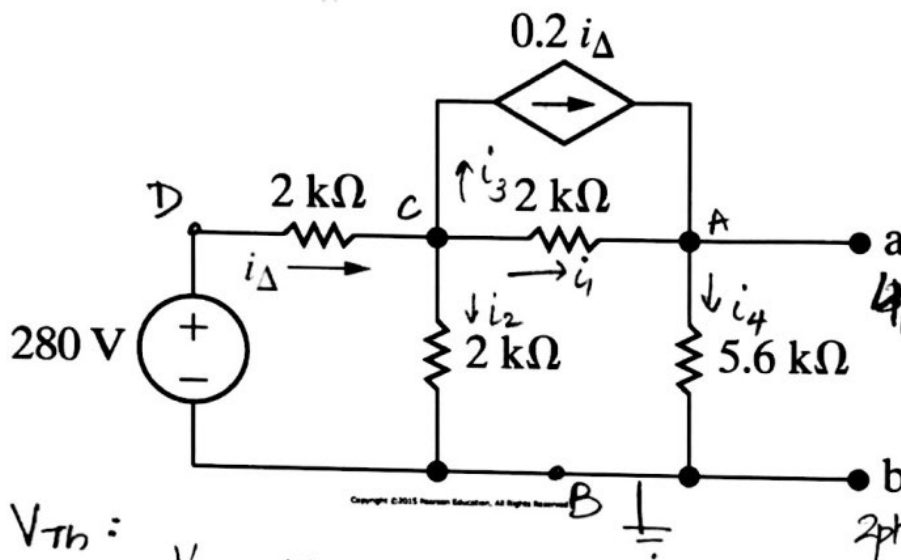

$V_{th} =$ _____

$R_{th} =$ _____

$I_N =$ _____

$R_N =$ _____

$P_{max} = 1.68W$

Finding V_{Th} :

$V_{Th} = V_{OC} = V_A$

3pts Given: $i_{\Delta} = \frac{V_D - V_C}{2k}$ & $V_D = 280V$

KCL @ C $\rightarrow -i_{\Delta} + i_1 + i_2 + i_3 = 0$



3pts $-\left(\frac{280 - V_C}{2k}\right) + \frac{V_C - V_A}{2k} + \frac{V_C}{2k} + 0.2i_{\Delta} = 0$

$\Rightarrow V_C - 280 + V_C - V_A + V_C + 0.2(280 - V_C) = 0$

$\Rightarrow -V_A + 2.8V_C = 224$ — (1)

KCL @ A $\rightarrow -0.2i_{\Delta} - i_1 + i_4 = 0$

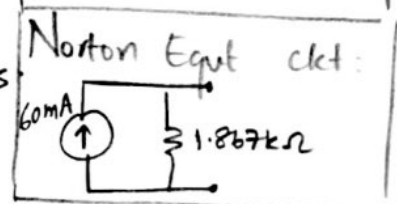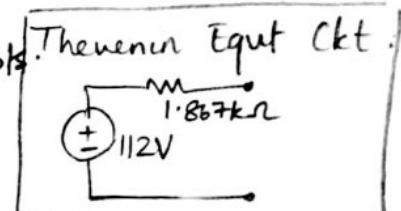3pts $\Rightarrow -0.2\left(\frac{280 - V_C}{2k\Omega}\right) - \left(\frac{V_C - V_A}{2k}\right) + \frac{V_A}{5.6k} = 0$



Page intentionally left blank. You may use this page for your work.


$$\Rightarrow -56 + \frac{0.2V_C - V_C + V_A}{2k} + \frac{V_A}{5.6k} = 0$$

$$\Rightarrow -56 \times 2.8 - 0.8V_C \times 2.8 + 3.8V_A = 0 \Rightarrow 3.8V_A - 2.24V_C = 156.8 \quad \text{--- (2)}$$

$$\Rightarrow V_A = \underline{112V} \quad \& \quad V_C = \underline{120V}$$

$$\Rightarrow V_{Th} = V_A = \underline{112V}$$

Finding R_{Th} :

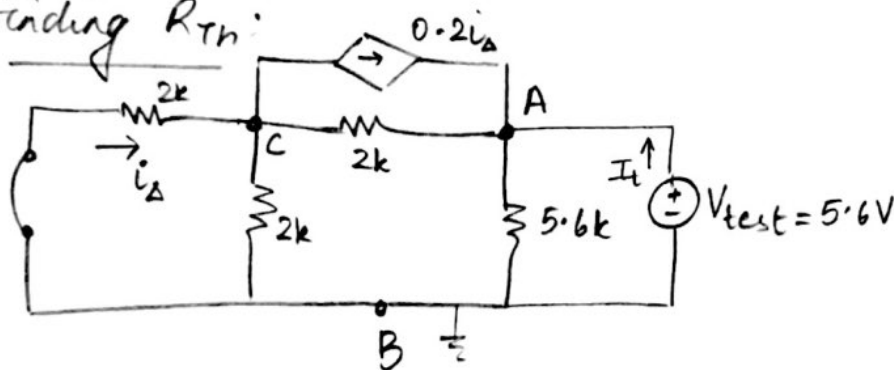

$$i_A = -\frac{V_C}{2k}$$

3pts. KCL @ C $\rightarrow \frac{V_C}{2k} + 0.2\left(-\frac{V_C}{2k}\right) + \frac{V_C}{2k} + \frac{V_C - 5.6V}{2k} = 0$


$$\Rightarrow 2.8V_C = 5.6V$$

$$\Rightarrow V_C = 2V$$

$$I_{test} = \frac{V_A}{5.6k} + \frac{V_A - V_C}{2k} - 0.2\left(-\frac{V_C}{2k}\right)$$


$$= \frac{5.6V}{5.6k} + \frac{5.6 - 2}{2k} + 0.2 \times \frac{2}{2k} = 1 + 1.8 + 0.2 = +3mA \quad \text{3pts.}$$
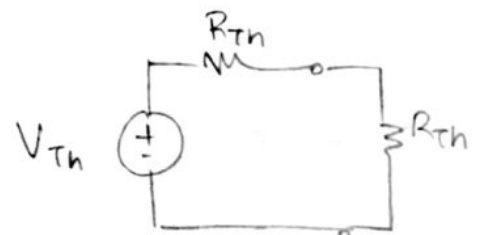
$$\Rightarrow R_{Th} = \frac{V_{Test}}{I_{Test}} = \frac{5.6V}{3mA} = \underline{1.867k\Omega}$$



4pts \Rightarrow max power transfer $= \frac{V_{Th}^2}{4R_{Th}} = \frac{112^2}{4 \times 1867} = \underline{1.68W}$

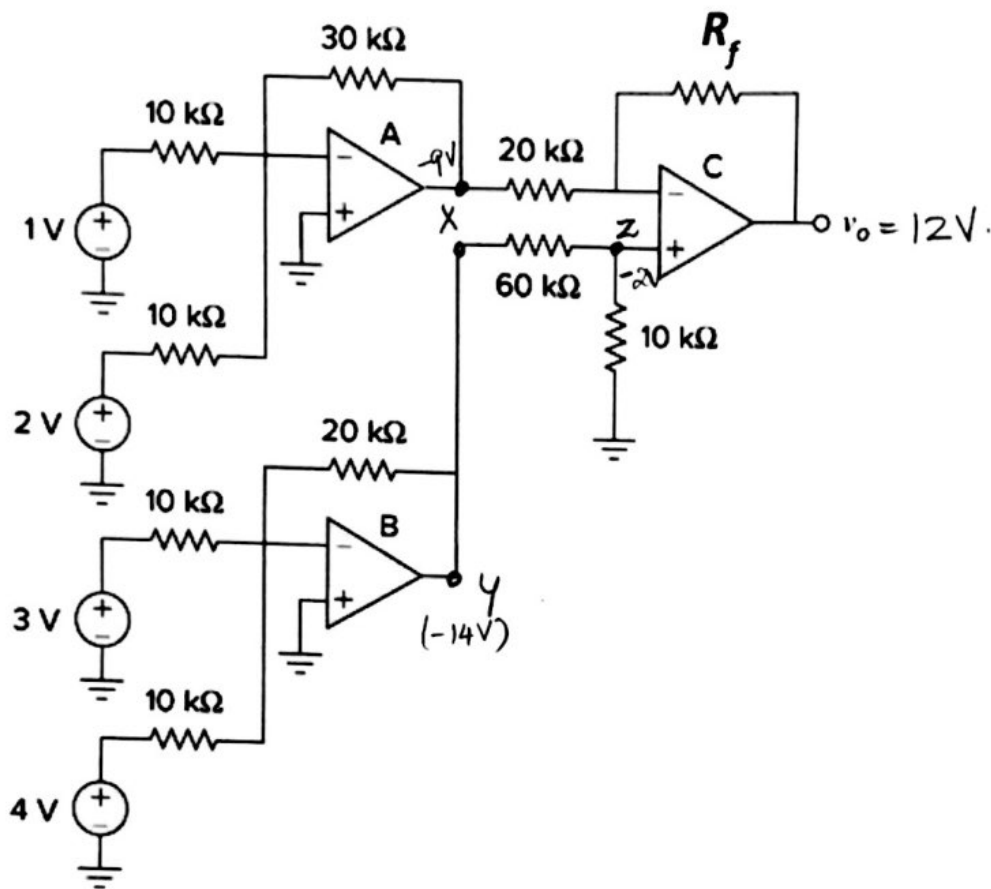3. Given that all the op-amps in the following circuit are ideal, what value of feedback resistor (R_f) will produce an output of 12V? [25 points]



$$R_f = \underline{40 \text{ k}\Omega}$$

5pts. $V_x = 1V\left(-\frac{30}{10}\right) + 2V\left(-\frac{30}{10}\right) = -3 - 6 = \underline{\underline{-9V}}$

5pts. $V_y = 3V\left(-\frac{20}{10}\right) + 4V\left(-\frac{20}{10}\right) = -6 - 8 = \underline{\underline{-14V}}$

5pts. $\Rightarrow V_z = V_{10k\Omega} = V_y \left(\frac{10k}{70k} \right) = -14 \times \frac{1}{7} = \underline{\underline{-2V}}$

$$i_{20k} = i_{R_f}$$

5pts. $\Rightarrow \frac{V_x - V_z}{20k} = \frac{V_z - V_o}{R_f} \Rightarrow \frac{-9 - (-2)}{20k} = \frac{-2 - 12}{R_f}$

Page intentionally left blank. You may use this page for your work.

$$\Rightarrow R_f = \frac{-14}{-7} \times 20k \cdot$$

$$= +2 \times 20k \cdot$$


if they work it correctly from their prev. equation)

$$5pts = \underline{\underline{40k\Omega}}$$


4. For the circuit shown below, all the capacitances are given in μF .

A. Find the equivalent capacitance between terminals a & b, as seen by the voltage source. [10 points]

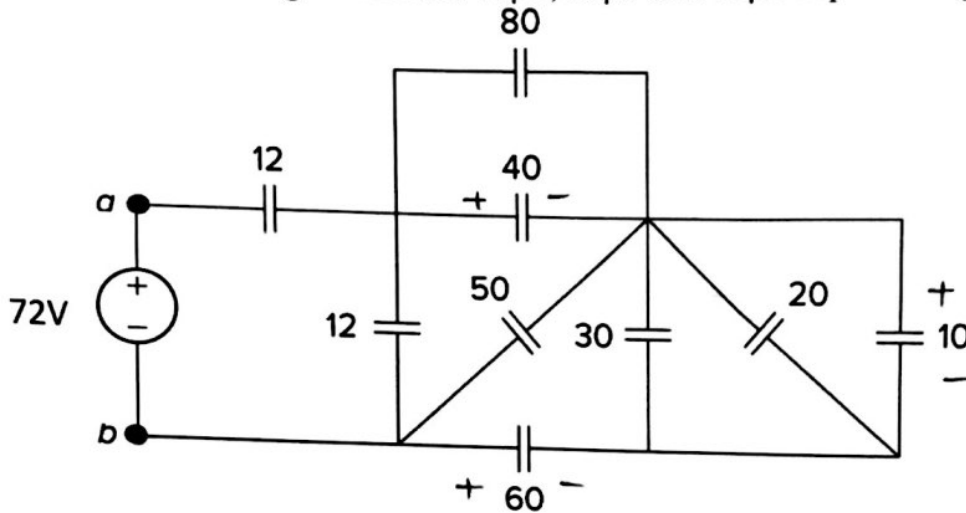B. Find the voltage across the $40\mu\text{F}$, $60\mu\text{F}$ and $10\mu\text{F}$ capacitors. [15 points]



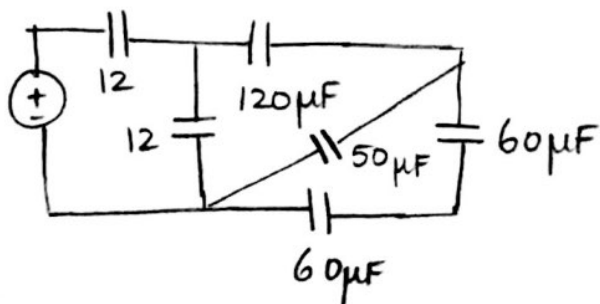2pts $10 \parallel 20 \parallel 30 = 60\mu\text{F}$
 $80 \parallel 40 = 120\mu\text{F}$






~~$C_{eq} = 10\mu\text{F}$~~
 $C_{eq} = 10\mu\text{F}$
 $V_{40\mu\text{F}} = 4.8\text{V}$
 $V_{60\mu\text{F}} = 3.6\text{V}$
 $V_{10\mu\text{F}} = 3.6\text{V}$

2pts 60 in series with $60\mu\text{F} = 30\mu\text{F}$

2pts $30 \parallel 50 = 80\mu\text{F}$

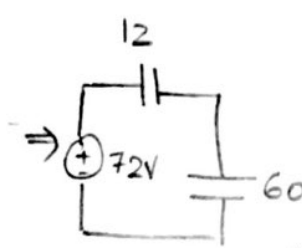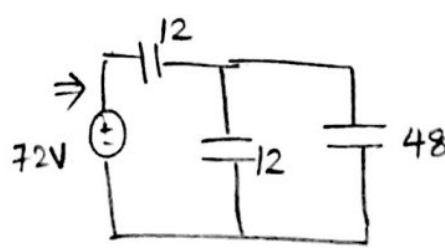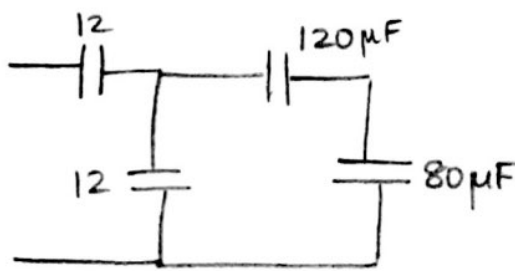$\frac{1}{120} + \frac{1}{80} = \frac{1}{48}$ 2pts



2pts $\Rightarrow C_{eq} = 10\mu\text{F}$
D. Nair

Page intentionally left blank. You may use this page for your work.

$$V_{60\mu F} = 72 \left(\frac{10\mu F}{60\mu F} \right)$$

$$\text{3pts} \cdot = \underline{\underline{12V}}$$

$$\text{3pts} \cdot V_{80\mu F} = 12V \left(\frac{48}{80} \right) = \underline{\underline{7.2V}}$$

$$\text{3pts} \rightarrow V_{120\mu F} = 12V \left(\frac{48}{120} \right) = \underline{\underline{4.8V}}$$

$$\downarrow V_{40\mu F} = V_{120\mu F} = \underline{\underline{4.8V}}$$

$$\text{3pts} \cdot V_{60\mu F} = 7.2V \left(\frac{30}{60} \right) = \underline{\underline{3.6V}}$$

$$\text{3pts} \cdot V_{10\mu F} = V_{60\mu F} = \underline{\underline{3.6V}}$$

$$V_C = V_{total} \left(\frac{C_{eq}}{C_1} \right)$$

5. Complete the following statements or state whether they are true or false: [Bonus 5 points]

- A. Inductor stores energy in its magnetic field.
- B. Voltage cannot change instantly for a capacitor.
- C. Inductance (L) is proportional to the number of turns (N) in the coil. (True False)
- D. You want to build an ideal step-down transformer rated 240/120Vrms. If the primary has 100 turns, how many turns should the secondary have? 50 turns
- E. What is the energy stored in a 60μF capacitor if it has a 3.6V across it?

$$\begin{aligned}
 W &= \frac{1}{2} CV^2 \\
 &= \frac{1}{2} \times 60\mu \times 3.6^2 \\
 &= \underline{\underline{0.388 \text{ mJ.}}}
 \end{aligned}$$